
Dynamic Analysis of the MCP16301 Switch Mode Power Converter Utilizing the MCP16301 Design Analyzer

INTRODUCTION

In a general sense, a power converter can be defined as a device which converts one form of energy into another on a continuous basis. Any storage or loss of energy within such a system while it is performing its conversion function is usually identical to the process of energy translation. There are many types of devices which can provide such a function with varying degrees of cost, reliability, complexity, and efficiency.

The mechanisms for power conversion can take many basic forms, such as those that are mechanical, electrical, or chemical processing in nature. This application note focuses on an inductor based, dc-dc switch mode power converter, the MCP16301. This power converter performs energy translation electrically and in a dynamic fashion. The dynamic behavior directly determines or influences four of the important characteristics of a switch mode power converter:

- Stability of the feedback loop
- Rejection of input voltage ripple and the closely related transient response to input voltage perturbations
- Output impedance and the closely related transient response to load perturbations
- Compatibility with an input EMI filter

Due to the complexity of the operation of a switch mode power converter, predicting its dynamic behavior is not always an easy task. Without accurate predictions, and depending only on building the circuit and performing component iterations until the operation is satisfactory, the engineering cost can easily escalate, schedules can be missed, and the final solution is rarely optimized.

BACKGROUND

The goal of this application note is to provide the analytical tools required to predict the dynamic behavior of the MCP16301 switch mode power converter. The dynamic analysis presented is basically a low-frequency, small-signal analysis, accurate at frequencies up to one-third of the switching frequency.

The validity can be extended toward higher frequencies, up to the Nyquist limit of one-half of the switching frequency, by employing a limited discrete time analysis correction factor. In its purest form, discrete time analysis is accurate and applicable both in large and small signal analysis. The penalty is rather complex difference equations and z-domain transfer functions with an absence of physical insight that is so essential in practice. Without the complexity, the small-signal analysis presented can be used to accurately predict, at all dc operating points, (1) the margin of stability of the converter, against closed loop oscillation, and (2) the frequency-domain and time-domain responses to perturbations in the input voltage and/or the output current. Large-signal analysis requires a different set of tools and is beyond the scope of this application note.

The MCP16301 employs a peak current mode control architecture, wherein, a control reference is used to regulate the peak current of the converter directly, simplifying the dynamics of the converter. The inner current loop essentially turns the inductor into a voltage controlled current source, reducing the control-to-output transfer function to a simple single-pole model of a current source feeding a capacitor. However, under certain operating conditions, the current feedback loop can become unstable, and the simple single-pole model cannot predict this event. It has been shown in [1] that a simple extension to the single pole model can be made that accounts for the subharmonic oscillation phenomenon seen in current-mode controlled converters. An approximation to discrete time analysis is combined with the simplicity of pole-zero representation to accurately model the oscillation phenomenon, ramp addition, and control-to-output transfer function.

Reference [1] provides the theoretical background, providing an exhaustive analysis of the buck converter with its associated models and results for fixed frequency, continuous conduction mode operation. In summary, the approximate control-to-output transfer function for the MCP16301 buck converter is given by:

$$\frac{\hat{v}_o}{\hat{v}_c} = \frac{R}{R_i} \frac{1}{1 + \frac{RT_s}{L} [m_c D' - 0.5]} F_p(s) F_h(s)$$

where

$$F_p(s) = \frac{1 + sCR_c}{1 + \frac{s}{\omega_p}}$$

where

$$\omega_p = \frac{1}{CR} + \frac{T_s}{LC}[m_c D' - 0.5]$$

and

$$F_h(s) = \frac{1}{1 + \frac{s}{\omega_n Q} + \frac{s^2}{\omega_n^2}}$$

where

$$\omega_n = \frac{\pi}{T_s}$$

where

$$Q = \frac{1}{\pi[m_c D' - 0.5]}$$

It is interesting that the discrete time approximation, $F_h(s)$, is common to all converters. The Q in the equation is controlled by the choice of the added slope compensation ramp. The MCP16301 employs a fixed slope compensation ramp.

Therefore, for different output voltages, it is necessary to change the inductor value to ensure the Q of the double pole is one or less, preventing gain peaking at one-half the switching frequency and subsequent subharmonic oscillation.

The slope compensation ramp factor is given by

$$m_c = 1 + \frac{S_e}{S_n}$$

where the slope compensation ramp slope, S_e , is

$$S_e = \frac{V_{PP}}{T_s}$$

and the slope of the sensed current waveform into the PWM controller, S_n , is

$$S_n = \frac{V_{ON} R_i}{L}$$

Setting $Q = 1$ and solving, the amount of slope compensation ramp necessary can be determined. This is usually expressed in terms of the inductor current off-time ramp slope, S_f , as opposed to the inductor current on-time ramp slope, S_n . Solving the equation in terms of S_f yields

$$\frac{S_e}{S_f} = 1 - \frac{0.18}{D}$$

where

$$S_f = \frac{V_{OFF} R_i}{L}$$

and

$$S_n = S_f \frac{D'}{D}$$

The appropriate inductor value can then be determined.

This is different than other suggestions. Some recommend adding as much ramp as the downslope. This is more than is needed, overdamping the system. For the buck converter, in theory, adding one half the downslope cancels all perturbations from input-to-output. In practice, this nulling is never achieved completely, and a small amount of noise makes it impossible.

MCP16301 DESIGN ANALYZER

Design Analyzer Input

The control-to-output transfer function is very useful for design purposes. The MCP16301 Design Analyzer employs all equations necessary to model the dynamic behavior of the converter and predict its response.

Referring to [Figure 1](#), the MCP16301 Design Analyzer is a tool for the designer to quickly and accurately access the stability, efficiency, and margin of the system at various operating conditions. Recommended passive component values are provided. The designer also has the ability to try alternative component values and access their effect on the system. The designer simply enters their operating system parameters of interest and verifies the output.

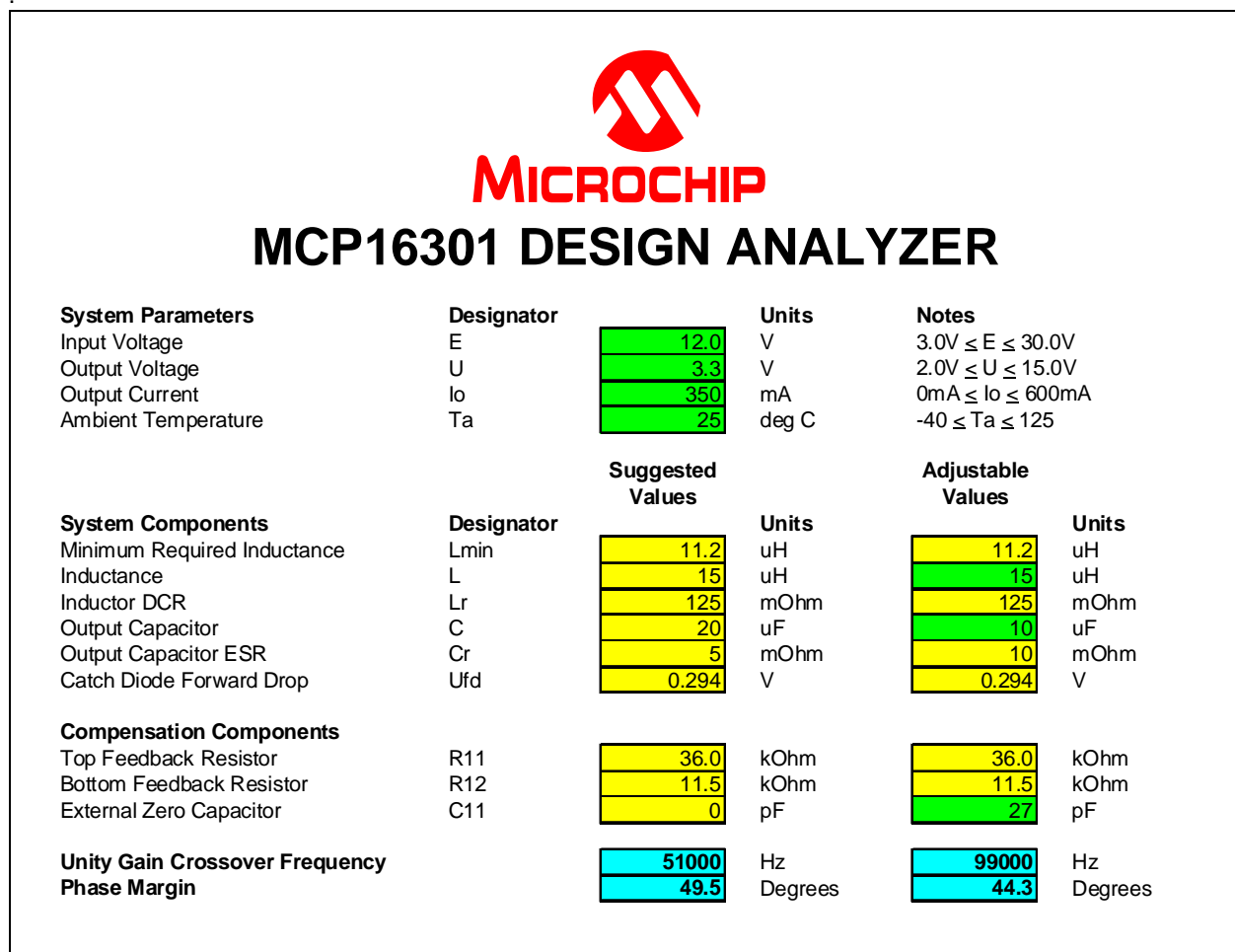


FIGURE 1: MCP16301 Design Analyzer User Inputs - Green.

Design Analyzer Output - Bode Plot

The Bode plot is a method of displaying complex values of circuit gain or impedance. The gain magnitude in dB is plotted versus log frequency. The phase angle is plotted separately against the same log frequency scale.

Bode plots are an excellent tool for analyzing switching power supply closed loop systems. The Bode plot provides good visibility into the gain and phase characteristics of the various loop elements. Calculation of the overall loop is made simply by adding gain in dB and phase in degrees.

Bode's theorem for simple systems, which includes most switching power supplies, states that the phase angle of the gain at any frequency is dependent upon the rate of change of gain magnitude versus frequency.

At this point, some important terms relative to stability analysis are defined:

- **Gain Margin**

Defined as the difference between unity gain (zero dB) and the actual gain when the phase reaches 180°. The recommended value is -6 dB to -12 dB.

- **Phase Margin**

Defined as the difference between 180° and the actual phase when the gain reaches unity gain. The recommended value is 45° to 60° .

- **Stability Criteria**

A commonly used derivative from the above two definitions, in accordance with Bode's theorem, is that if the slope of the gain response as it crosses the unity-gain axis is not more than -6 dB/octave, the phase margin will be greater than 45° and the system will be stable.

No approximations have been made in the Design Analyzer other than those required for linearizing the system. It should be understood that phase shift is caused not only by reactive components, but also by time delay, such as transistor storage time or hold time in a sampling system. Switch delays normally have little effect as long as there is no explicit sample-and-hold function, and the frequencies of interest are well below the switching frequency. For example, the effect of a $1 \mu\text{s}$ delay in a 100 kHz system is a phase shift of less

than 4° . There will also be potential phase lags due to the op amp and parasitic components. Thus, although technically a second-order system could potentially be stable since 180° phase lag is only asymptotically approached, we can expect that this system, as currently defined, will be unstable in practice and, in any case, would suffer serious ringing under any external disturbance.

Figure 2 depicts a Bode plot output example from the Design Analyzer. The S_Gain and S_Phase plots represent the overall system loop with the suggested component values. The A_Gain and A_Phase curves represent the overall system loop with the actual system component values.

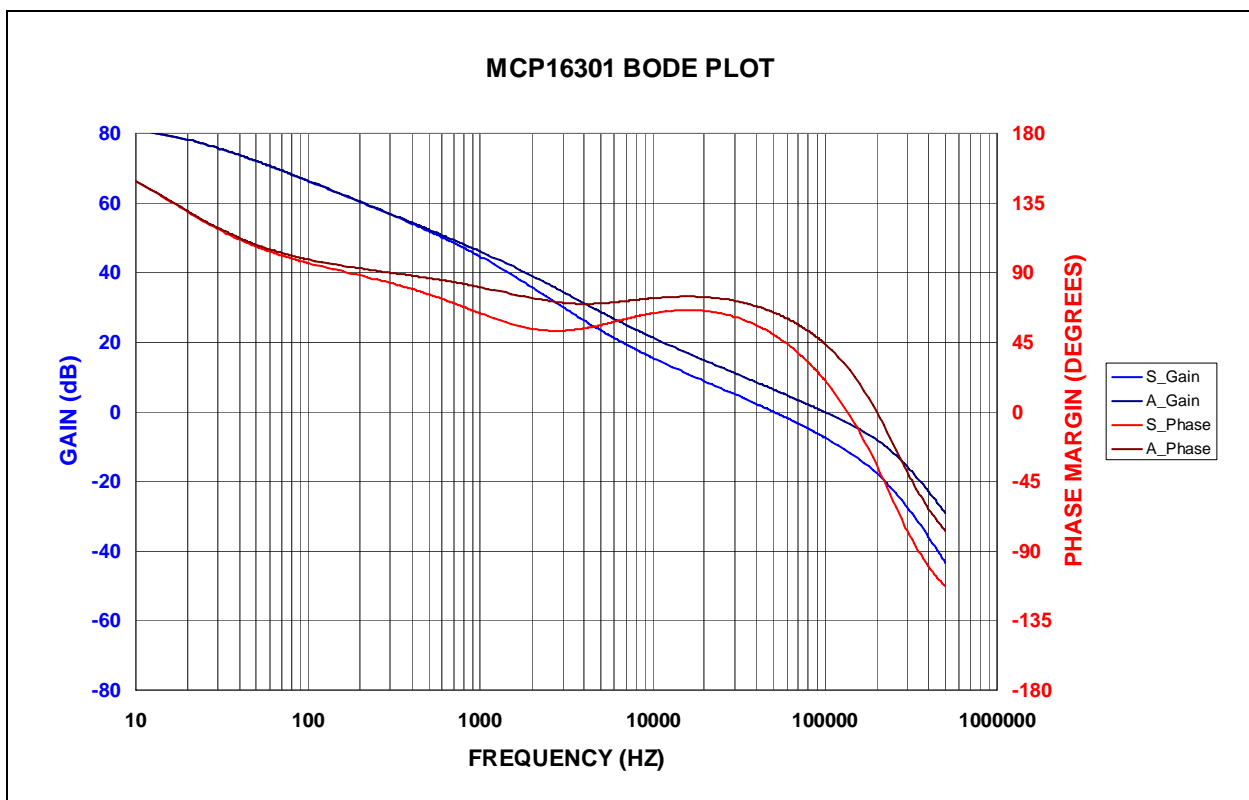


FIGURE 2: MCP16301 Design Analyzer Bode Plot Output.

Design Analyzer Output - Efficiency

Switch mode power converters employ a restricted set of components which include inductors, capacitors, transformers, switches, and resistors. How these circuit components are connected is determined by the desired power translation. Resistors introduce

undesirable power loss. Since high efficiency is usually an overriding requirement in most applications, resistive circuit elements should be avoided or minimized. Only on rare occasions and for very specific reasons are power consuming resistances introduced into the main power control path. In auxiliary circuits,

such as sequence, monitor, and control electronics of total system, high value resistors are common place, since their loss contributions are usually insignificant.

The Design Analyzer provides the calculated efficiency of power conversion implemented with the suggested component values. Figure 3 depicts an Efficiency versus Output Current graph example.

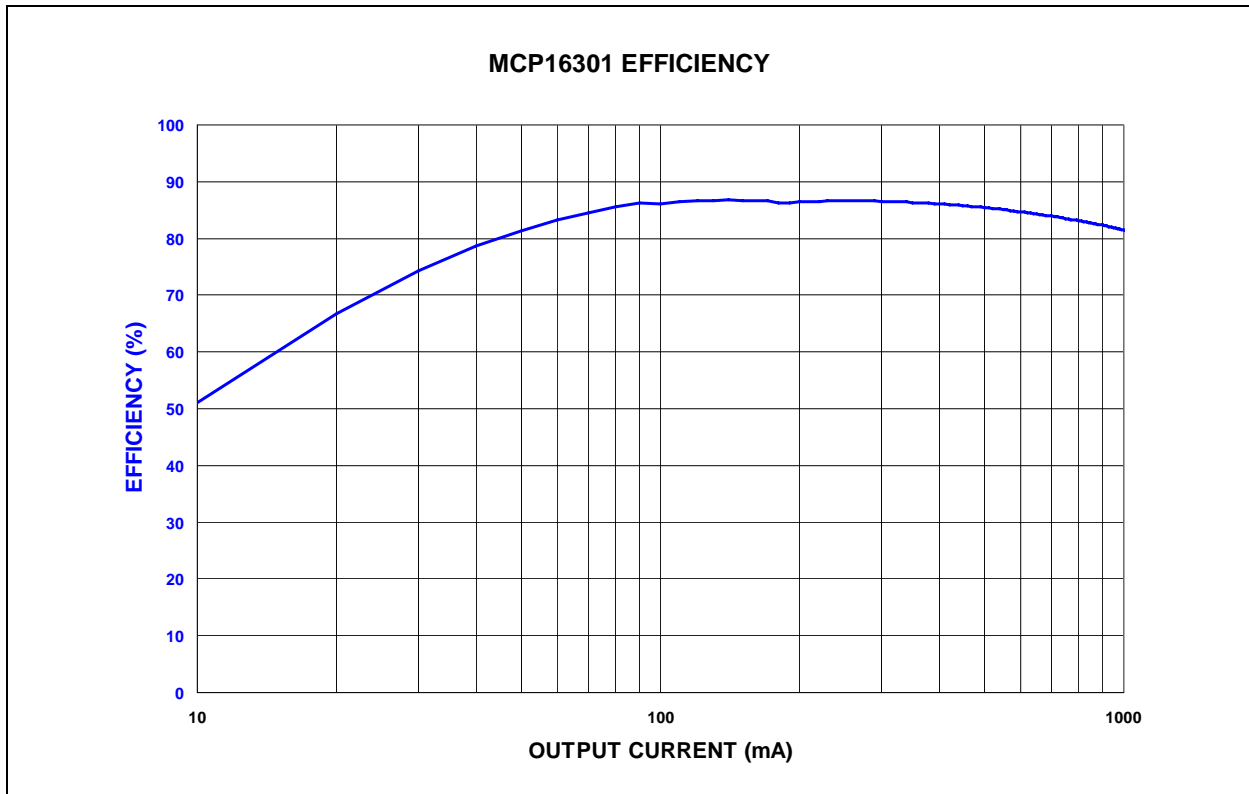


FIGURE 3: MCP16301 Design Analyzer Efficiency vs Output Current.

SUMMARY

The MCP16301 Design Analyzer provides the designer with a tool to analyze the dynamic behavior of the MCP16301 Buck Converter. It accurately predicts the dynamic operation, reducing the engineering cost, schedule times, and hones in on an optimized final solution. However, the Design Analyzer should not be considered a substitute for proper in-system verification and validation.

REFERENCES

- Ridley, R.B., "A New, Continuous-Time Model For Current-Mode Control", IEEE Transactions on Power Electronics, Vol. 6, Issue 2, pp. 271-280, 1991.
- Sheehan, R., "Emulated Current Mode Control for Buck Regulators Using Sample and Hold Technique", Power Electronics Technology Exhibition and Conference, PES02, October 2006.
- Dixon, L.H., "Closing the Feedback Loop", Appendix C, Unitrode Power Supply Design Seminar, pp. 2C1 - 2C18, 1983.
- Vorperian, V., *Fast Analytical Techniques for Electrical and Electronic Circuits*, Cambridge, UK: Cambridge University Press, 2002.
- Kislovski, A., Redl, R., and Sokal, N., *Dynamic Analysis of Switching-Mode DC/DC Converters*, Lexington, MA: Design Automation, Inc., 2003.
- Astrom, K., and Wittenmark, B., *Computer Controlled Systems: Theory and Design, Third Edition*, Upper Saddle River, NJ: Prentice Hall, Inc., 1997.
- Severns, R., and Bloom, G., *Modern DC-to-DC Switchmode Power Converter Circuits*, New York, NY: Van Nostrand Reinhold Company, Inc., 1985.

NOTES:

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable.”

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, KEELOQ, KEELOQ logo, MPLAB, PIC, PICmicro, PICSTART, PIC³² logo, rPIC and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


FilterLab, Hampshire, HI-TECH C, Linear Active Thermistor, MXDEV, MXLAB, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, dsSPEAK, ECAN, ECONOMONITOR, FanSense, HI-TIDE, In-Circuit Serial Programming, ICSP, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, mTouch, Omniscient Code Generation, PICC, PICC-18, PICDEM, PICDEM.net, PICkit, PICTail, REAL ICE, rLAB, Select Mode, Total Endurance, TSHARC, UniWinDriver, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2011, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

ISBN: 978-1-61341-177-3

Microchip received ISO/TS-16949:2002 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.

**QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==**

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland
Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

Santa Clara
Santa Clara, CA
Tel: 408-961-6444
Fax: 408-961-6445

Toronto
Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office
Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2401-1200
Fax: 852-2401-3431

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8569-7000
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Chongqing
Tel: 86-23-8980-9588
Fax: 86-23-8980-9500

China - Hangzhou
Tel: 86-571-2819-3180
Fax: 86-571-2819-3189

China - Hong Kong SAR
Tel: 852-2401-1200
Fax: 852-2401-3431

China - Nanjing
Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

China - Xiamen
Tel: 86-592-2388138
Fax: 86-592-2388130

China - Zhuhai
Tel: 86-756-3210040
Fax: 86-756-3210049

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444
Fax: 91-80-3090-4123

India - New Delhi
Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune
Tel: 91-20-2566-1512
Fax: 91-20-2566-1513

Japan - Yokohama
Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Daegu
Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur
Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang
Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-6578-300
Fax: 886-3-6578-370

Taiwan - Kaohsiung
Tel: 886-7-213-7830
Fax: 886-7-330-9305

Taiwan - Taipei
Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

UK - Wokingham
Tel: 44-118-921-5869
Fax: 44-118-921-5820